

<b>Course Name:</b>	<b>Digital Design Laboratory</b>	<b>Semester:</b>	<b>III</b>
<b>Date of Performance:</b>	<b>21 / 08 / 2023</b>	<b>Batch No:</b>	<b>C-2</b>
<b>Faculty Name:</b>		<b>Roll No:</b>	<b>16010122266</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	<b>___/25</b>

**Experiment No: 4**  
**Title: 4-bit magnitude comparator**

**Aim and Objective of the Experiment:**

To design a 2-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

**COs to be achieved:**


**CO2:** Use different minimization technique and solve combinational circuits.

**Tools used:**

Trainer kits

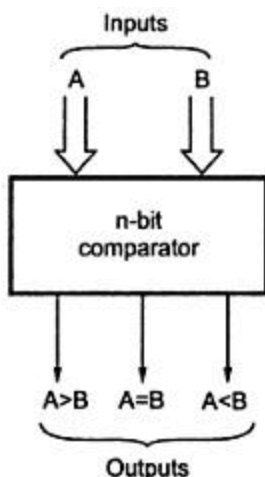**Theory:**

**Comparator:** The comparison of two numbers is an operator that determines one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$  (or)  $A < B$ .



## Two Bit Magnitude Comparator Implementation Details:

### Truth Table from the Truth Table:

INPUT				OUTPUT		
A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

16010122266 PKmath


$$(A < B) = A_1' B_1 + A_0' B_1 B_0 + A_1' A_0' B_0$$

$$(A = B) = A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0' B_1 B_0' + A_1 A_0 B_1 B_0$$

$$= (A_0 \text{ XNOR } B_0) (A_1 \text{ XNOR } B_1)$$


$$(A > B) = A_1 B_1' + A_0 B_1' B_0' + A_1 A_0 B_0'$$

### Logic Diagram of 2-bit Comparator

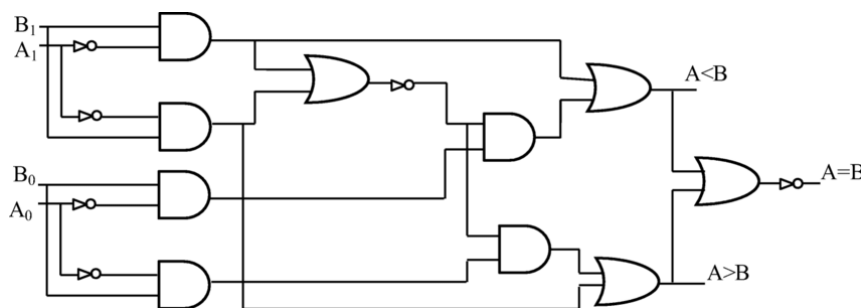


## Four Bit Magnitude Comparator Implementation Details

### Pin Diagram of IC 7485

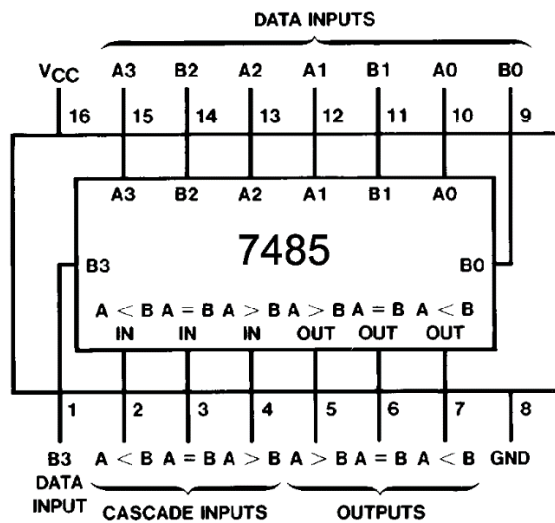

### Logic Diagram of IC 7485

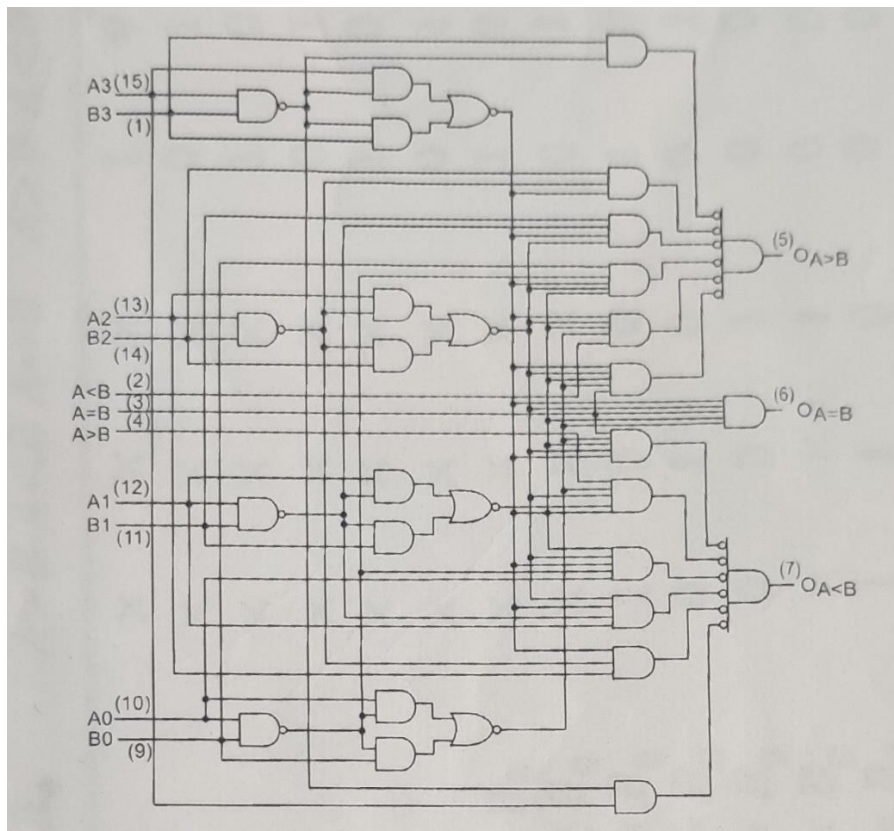

## Comparing Table

TRUTH TABLE									
COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A <sub>3</sub> ,B <sub>3</sub>	A <sub>2</sub> ,B <sub>2</sub>	A <sub>1</sub> ,B <sub>1</sub>	A <sub>0</sub> ,B <sub>0</sub>	I <sub>A</sub> >B	I <sub>A</sub> <B	I <sub>A</sub> =B	O <sub>A</sub> >B	O <sub>A</sub> <B	O <sub>A</sub> =B
A <sub>3</sub> >B <sub>3</sub>	X	X	X	X	X	X	H	L	L
A <sub>3</sub> <B <sub>3</sub>	X	X	X	X	X	X	L	H	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> >B <sub>2</sub>	X	X	X	X	X	H	L	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> <B <sub>2</sub>	X	X	X	X	X	L	H	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> >B <sub>1</sub>	X	X	X	X	H	L	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> <B <sub>1</sub>	X	X	X	X	L	H	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> >B <sub>0</sub>	X	X	X	H	L	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> <B <sub>0</sub>	X	X	X	L	H	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> =B <sub>0</sub>	H	L	L	H	L	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> =B <sub>0</sub>	L	H	L	L	H	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> =B <sub>0</sub>	X	X	H	L	L	H
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> =B <sub>0</sub>	H	H	L	L	L	L
A <sub>3</sub> =B <sub>3</sub>	A <sub>2</sub> =B <sub>2</sub>	A <sub>1</sub> =B <sub>1</sub>	A <sub>0</sub> =B <sub>0</sub>	L	L	L	H	H	L

H = HIGH Level  
 L = LOW Level  
 X = IMMATERIAL

## Implementation Details

### Procedure:

- 1) Locate the IC 7485 on the trainer kit.
- 2) Connect 1<sup>st</sup> input no. to A<sub>3</sub>-A<sub>0</sub> input slot and 2<sup>nd</sup> to B<sub>3</sub>-B<sub>0</sub>.
- 3) Connect the output Y<sub>A>B</sub>, Y<sub>A<B</sub> and Y<sub>A=B</sub> to the output indicators.
- 4) Switch ON the power supply and monitor the output for various input combinations.

## Post Lab Subjective/Objective type Questions:

1. Give some applications of magnitude comparator.

Some applications of magnitude comparator are: -

- Comparators are used in central processing units (CPUs) and microcontrollers (MCUs).
- These are used in control applications in which the binary numbers representing physical variables such as temperature, position, etc. are compared with a reference value.
- Comparators are also used as process controllers and for Servo motor control.
- Used in password verification and biometric applications.
- Used to address decoding circuitry in computers.

