



Counters

- ✓ **Counters** are sequential circuits which "count" through a specific state sequence.
 - They can count up, count down, or count through other fixed sequences.
- ✓ Two distinct types are in common usage:
 - Ripple Counters
 - Clock connected to the flip-flop clock input on the LSB bit flip-flop
 - For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous!
 - Output change is delayed more for each bit toward the MSB.
 - Resurgent because of low power consumption
 - Synchronous Counters
 - Clock is directly connected to the flip-flop clock inputs
 - Logic is used to implement the desired state sequencing

Ripple Counter

✓ How does it work?

  - When there is a **positive edge** on the clock input of **A**, **A** **complements**
- The **clock input** for flip-flop **B** is the **complemented output** of flip-flop **A**
- When flip **A** **changes from 1 to 0**, there is a **positive edge** on the clock input of **B** causing **B** to **complement**




Ripple Counter (continued)

- ✓ The arrows show the cause-effect relationship from the prior slide

- ✓ The corresponding sequence of states \Rightarrow

$$(B,A) = (0,0), (0,1), (1,0), (1,1), (0,0), (0,1), \dots$$

 - ✓ Each additional bit, C, D, ...behaves like bit B, changing half as frequently as the bit before it.
- ✓ For 3 bits: $(C,B,A) = (0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0), (1,1,1), (0,0,0), \dots$




Ripple Counter (continued)

- ✓ These circuits are called **ripple counters** because each edge sensitive transition (positive in the example) causes a change in the **next flip-flop's state**.
- ✓ The **changes ripple upward** through the chain of flip-flops, i. e., each transition occurs after a clock-to-output **delay** from the stage before.

Ripple Counter (continued)


✓ Starting with $C = B = A = 1$, equivalent to $(C,B,A) = 7$ base 10, the next clock increments the count to $(C,B,A) = 0$ base 10. In fine timing detail:

 - The clock to output delay t_{PHL} causes an increasing delay from clock edge for each stage transition.
- Thus, the count “ripples” from least to most significant bit.
- For n bits, total worst case delay is $n t_{PHL}$.



Synchronous Counters

 - ✓ To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- ✓ For an up-counter, use an **incrementer** ⇒



Other Counters

✓ Counters:

- **Down Counter** - counts downward instead of upward
- **Up-Down Counter** - counts up or down depending on value a control input such as Up/Down
- **Parallel Load Counter** - Has parallel load of values available depending on control input such as Load

✓ Divide-by-n (Modulo n) Counter

- Count is remainder of division by n ; n may not be a power of 2
- Count is arbitrary sequence of n states specifically designed state-by-state
- Includes modulo 10 which is the **BCD counter**

Design Example: Synchronous BCD

- ✓ Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- ✓ Input combinations 1010 through 1111 are don't cares

Current State				Next State			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

Synchronous BCD (continued)

- ✓ Use **K-Maps** to two-level optimize the next state equations:

$$D1 = \overline{Q1}$$

$$D2 = \overline{Q8}\overline{Q2}Q1 + Q2\overline{Q1}$$

$$D4 = \overline{Q4}\overline{Q2}Q1 + Q4\overline{Q2} + Q4\overline{Q1}$$

$$D8 = Q8\overline{Q1} + Q4Q2Q1$$


- ✓ The logic diagram can be draw from these equations
 - An asynchronous or synchronous reset should be added
- ✓ What happens if the counter is perturbed by a power disturbance or other interference and it enters a state other than 0000 through 1001?

Synchronous BCD (continued)

- ✓ Find the actual values of the six next states for the don't care combinations from the equations
- ✓ Find the overall state diagram to assess behavior for the don't care states (states in decimal)


$$\begin{aligned}D1 &= \overline{Q1} \\ D2 &= \overline{Q8}Q2Q1 + Q2\overline{Q1} \\ D4 &= \overline{Q4}Q2Q1 + Q4\overline{Q2} + Q4\overline{Q1} \\ D8 &= Q8\overline{Q1} + Q4Q2Q1\end{aligned}$$

Present State	Next State
Q8 Q4 Q2 Q1	Q8 Q4 Q2 Q1
1 0 1 0	1 0 1 1
1 0 1 1	0 1 0 0
1 1 0 0	1 1 0 1
1 1 0 1	0 1 0 0
1 1 1 0	1 1 0 1
1 1 1 1	1 0 0 0

 

Counting Modulo 7: Synchronously Load on Terminal Count of 6

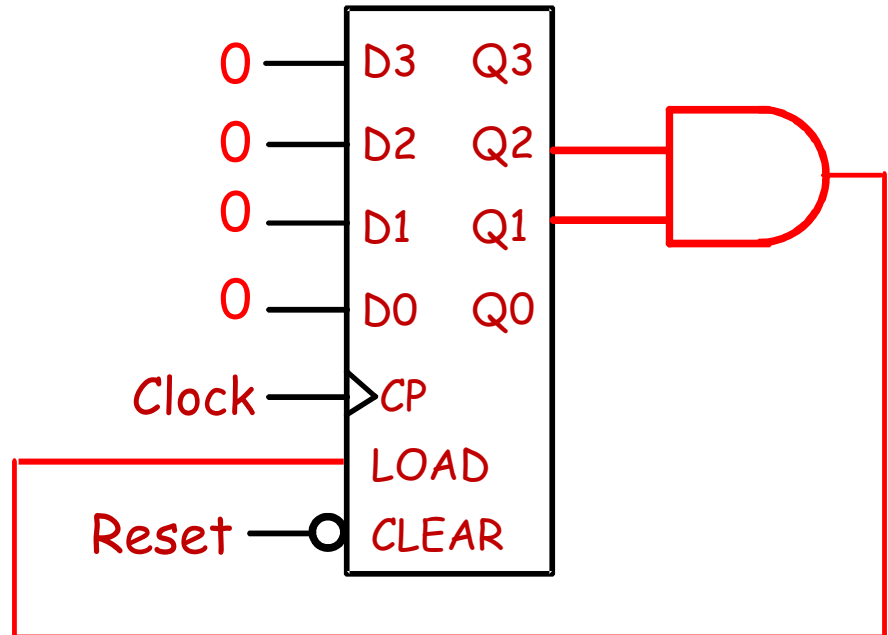
- ✓ A synchronous 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a Modulo 7 counter
- ✓ Use the Load feature to detect the count "6" and load in "zero". This gives a count of 0, 1, 2, 3, 4, 5, 6, 0, 1, 2, 3, 4, 5, 6, 0, ...
- ✓ Using don't cares for states above 0110



Counting Modulo 6: Synchronously Preset 9 on Reset and Load 9 on Terminal Count 14

- ✓ A synchronous, 4-bit binary counter with a synchronous Load is to be used to make a Modulo 6 counter.

 - ✓ Use the Load feature to preset the count to 9 on Reset and detection of count 14.



- ✓ This gives a count of 9, 10, 11, 12, 13, 14, 9, 10, 11, 12, 13, 14, 9, ...
- ✓ If the terminal count is 15 detection is usually built in as Carry Out (CO)

Example 4: Design a modulo-8 up-counter which counts in the way specified below, use J-K FF

Decimal	Gray
0	000
1	001
2	011
3	010
4	110
5	111
6	101
7	100

Example 4: TRUTH TABLE

present state

next state

Y_3	Y_2	Y_1	Y_{3+}	Y_{2+}	Y_{1+}
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

Example 4: Gray code counter

y3

	1	1	
y ₁		1	1

y₂

	1	x	x
		x	x

q-half q-half

$$J_{y_3} = y_2 \bar{y}_1$$

x	x		1
x	x		

$$K_{y_3} = \bar{y}_2 y_1$$

Example 4: Gray code counter

y_2

			y_3
		1	1
y_1	1	1	
		y_2	

			y_2
	1	x	x
		x	x
\bar{q} -half	q-half	\bar{q} -half	

$$J_{y_2} = \bar{y}_3 y_1$$

			y_2
x	x		1
x	x		

$$K_{y_2} = y_3 y_1$$

Example 4: Gray code counter

	y_3		
	1		1
y_1	1		1
		y_2	

y_1

	<div>1</div>		<div>1</div>		\bar{q} -half		x	<div>x</div>	x	<div>x</div>
y_1	<div>x</div>	x	<div>x</div>	x	q-half	y_1		<div>1</div>		<div>1</div>

$$J_{y1} = \bar{y}_3 \bar{y}_2 + y_3 y_2$$

$$K_{y1} = \bar{y}_2 y_3 + y_2 \bar{y}_3$$